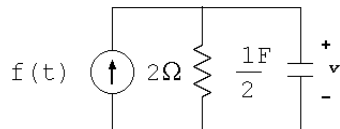


ECE210 / ECE211 - Homework 05

Solution

1. Consider the following circuit with $v(0^-) = 2\text{ V}$ and let $f(t) = \cos(\sqrt{3}t + \frac{\pi}{3})\text{ A}$, For $t > 0$, obtain:

Solution : Equivalent circuit shows below



The ODE for this system is obtained from a KCL at the top node as:

$$f(t) = \frac{v}{2} + i_c = \frac{v}{2} + C \frac{dv}{dt} = \frac{v}{2} + \frac{1}{2} \frac{dv}{dt} \rightarrow 2f(t) = \frac{dv}{dt} + v$$

The particular solution : $v_p(t) = A \cos(\sqrt{3}t) + B \sin(\sqrt{3}t)$

$$2 \cos(\sqrt{3}t + \frac{\pi}{3}) = \cos(\sqrt{3}t) - \sqrt{3} \sin(\sqrt{3}t) = \frac{dv_p}{dt} + v_p = A \cos(\sqrt{3}t) + B \sin(\sqrt{3}t) - A\sqrt{3} \sin(\sqrt{3}t) + B\sqrt{3} \cos(\sqrt{3}t)$$

Solving : $A = 1, B = 0$

Therefore, the particular solution is $V_p(t) = \cos(\sqrt{3}t)$

The homogeneous solution : $V_h(t) = K e^{-t/\tau}$

Here, $\tau = RC = 2\Omega \times \frac{1}{2}F = 1s$ is the RC time constant.

Fix the initial condition on the total solution, $V(t) = V_h(t) + V_p(t)$, hence

$$V(0^-) = 2 = K + 1$$

$$K = 1$$

The homogenous solution is $V_h(t) = e^{-t} V$.

- (a) the zero-state voltage across the capacitor's terminals, $v_{zs}(t)$,

Solution : The zero-state response must satisfy $v_{zs}(0) = 0$

$$V(0^-) = 0 = K + 1$$

$$K = -1$$

The zero-state solution is $v_{zs}(t) = -e^{-t} + \cos(\sqrt{3}t)\text{ V}$.

- (b) the zero-input voltage across the capacitor's terminals, $v_{zi}(t)$,

Solution :

$$\begin{aligned} \frac{dv(t)}{dt} + v(t) &= 0 \\ v &= C e^{-t} \end{aligned}$$

use initial condition we find $C = 2$

$$v_{zi}(t) = 2e^{-t}\text{ V}.$$

- (c) the transient voltage across the capacitor's terminals, $v_{tr}(t)$,

Solution : $v_{tr}(t) = e^{-t}\text{ V}$.

- (d) the steady state voltage across the capacitor's terminals, $v_{ss}(t)$,


Solution : $v_{ss}(t) = \cos(\sqrt{3}t)\text{ V}$.

- (e) the total voltage across the capacitor's terminals, $v(t)$.

Solution : The total voltage is $V(t) = \cos(\sqrt{3}t) + e^{-t}$ V.

Note that : $v(t) = v_p(t) + v_h(t) = v_{ZI}(t) + v_{ZS}(t) = v_{tr}(t) + v_{ss}(t)$

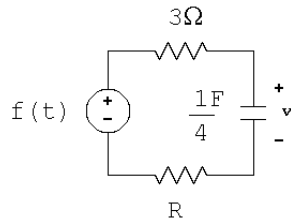2. Consider the following circuit with $f(t) = \frac{2}{\sqrt{3}}\cos(\omega t)$ volts and $v(0^-) = v_0$ volts.



It is known that for $t > 0$, $v(t) = Ae^{-t} + B \cos\left(\frac{1}{\sqrt{3}}t\right) + D \sin\left(\frac{1}{\sqrt{3}}t\right)$ volts.

- Write the ODE that governs this system for $t > 0$ in terms of R , $v(t)$, and ω .
- Find the value of R .
- What is the value of ω ?
- What are the values of B and D ?
- Identify $v_{tr}(t)$, the transient component of $v(t)$.
- Identify $v_{ss}(t)$, the steady-state component of $v(t)$.
- What is steady-state phasor V ?

Solution :

- $f(t) = v(t) + (3 + R)\frac{1}{4}\frac{dv}{dt}$
- $\tau = RC = 1s$, hence $R = 1\Omega$.
- $\omega = \frac{1}{\sqrt{3}}\text{rad/s}$.
- At steady state, the ODE in part (a) must be satisfied

$$\frac{2}{\sqrt{3}}\cos\left(\frac{1}{\sqrt{3}}t\right) = B\cos\left(\frac{1}{\sqrt{3}}t\right) + D\sin\left(\frac{1}{\sqrt{3}}t\right) - \frac{B}{\sqrt{3}}\sin\left(\frac{1}{\sqrt{3}}t\right) + \frac{D}{\sqrt{3}}\cos\left(\frac{1}{\sqrt{3}}t\right)$$

Solving : $B = \frac{\sqrt{3}}{2}$ and $D = \frac{1}{2}$.

- The transient component $v_{tr}(t) = Ae^{-t}$ V.
We fix the value of A using the initial condition $A + B = v_0$, hence, $A = v_0 - \frac{\sqrt{3}}{2}$
- The steady-state component is $v_{ss}(t) = B\cos\left(\frac{1}{\sqrt{3}}t\right) + D\sin\left(\frac{1}{\sqrt{3}}t\right)$ V, where B and D are solved in part (d)
- $V = B + De^{-j\frac{\pi}{6}} = e^{-j\frac{\pi}{6}}$

3. The different parts of this problem are unrelated:

- Express $\frac{e^{-j4t} - e^{j4t}}{j4}$ in terms of a cosine function.

Solution :

$$\frac{e^{-j4t} - e^{j4t}}{j4} = -\frac{1}{2}\sin(4t) = -\frac{1}{2}\cos\left(4t - \frac{\pi}{2}\right)$$

- Express $\frac{e^{-j3t} + e^{j3t}}{4}$ in terms of a sine function.

Solution :

$$\frac{e^{-j3t} + e^{j3t}}{4} = \frac{1}{2}\cos(3t) = \frac{1}{2}\sin\left(3t + \frac{\pi}{2}\right)$$

- (c) Express $\text{Re}\{2e^{j\frac{\pi}{3}}e^{-j5t}\}$ in terms of a cosine function.

Solution :

$$\text{Re}\{2e^{j\frac{\pi}{3}}e^{-j5t}\} = 2\cos(-5t + \frac{\pi}{3})$$

- (d) Determine the phasor F of $f(t) = -2\sin(2t - \frac{\pi}{3})$. Express F in both polar and rectangular coordinates.

Solution :

$$f(t) = -2\cos(2t - \frac{5\pi}{6})$$

the phasor is $F = 2e^{j\frac{\pi}{6}} = \sqrt{3} + j$

- (e) Determine the phasor F of $f(t) = \cos(3t - \frac{\pi}{2})$. Express F in both polar and rectangular coordinates.

Solution :

$$F = e^{-j\frac{\pi}{2}} = -j$$

- (f) Express the phasor $F = 2 - j2$ in terms of a cosine function $f(t)$ having frequency $\omega = 9 \frac{\text{rad}}{\text{s}}$.

Solution :

$$F = 2 - j2 = 2\sqrt{2}e^{-j\frac{\pi}{4}}$$

$$f(t) = 2\sqrt{2}\cos(9t - \frac{\pi}{4})$$

- (g) Express the phasor $F = 3e^{-j\frac{\pi}{3}}$ in terms of a cosine function $f(t)$ having frequency $\omega = 9 \frac{\text{rad}}{\text{s}}$.

Solution :

$$f(t) = 3\cos(9t - \frac{\pi}{3})$$

4. Determine the phasor F of the following cosinusoidal functions $f(t)$:

- (a) $f(t) = 2\cos(2t + \frac{\pi}{3})$.

Solution :

$$F = 2e^{j\frac{\pi}{3}}$$

- (b) $f(t) = A\sin(\omega t)$

Solution :

$$F = -Aj$$

- (c) $f(t) = -5\sin(\pi t)$

Solution :

$$F = 5j$$

5. Determine the cosine function $f(t)$ with frequency $\omega = 2\text{rad/s}$, corresponding to the following phasors :

- (a) $F = j2$

Solution :

$$f(t) = 2\cos(2t + \frac{\pi}{2})$$

- (b) $F = 3e^{-j\frac{\pi}{6}}$

Solution :

$$f(t) = 3\cos(2t - \frac{\pi}{6})$$

(c) $F = j2 + 3 e^{-j\frac{\pi}{6}}$

Solution :

$$F = j2 + 3 \left(\frac{\sqrt{3}}{2} - j\frac{1}{2} \right) = \frac{3\sqrt{3}}{2} + \frac{1}{2}$$

$$f(t) = \sqrt{7} \cos \left(2t + \tan^{-1} \left(\frac{1}{3\sqrt{3}} \right) \right)$$

6. Use the phasor method to determine amplitude and phase shift (in rad) of the following signals when written as cosines:

(a) $f(t) = 3 \cos(4t) - 4 \sin(4t)$

Solution :

$$F = 3 + 4j$$

$$= 5 e^{j \tan^{-1}(4/3)}$$

$$f(t) = 5 \cos \left(4t + \tan^{-1} \left(\frac{4}{3} \right) \right)$$

(b) $g(t) = 2 [\cos(wt) + \cos(wt + \frac{\pi}{4})]$

Solution :

$$G = 2 + 2e^{j\frac{\pi}{4}} = 2 + 2 \left(\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}} \right) = \frac{2}{\sqrt{2}}(\sqrt{2} + 1) + j\frac{2}{\sqrt{2}}$$

$$= 2\sqrt{2 + \sqrt{2}} e^{j \tan^{-1}(1/(\sqrt{2}+1))}$$

$$g(t) = 2\sqrt{2 + \sqrt{2}} \cos \left(wt + \tan^{-1} \left(\frac{1}{\sqrt{2} + 1} \right) \right)$$