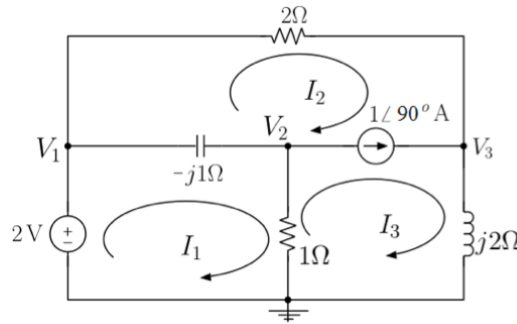


## ECE210 / ECE211 - Homework 6 Solution

1. In the following circuit determine the node-voltage phasors  $V_1$ ,  $V_2$ , and  $V_3$  and express them in polar form.



**Solution:**

$$\mathbf{V}_1 = 2 \text{ V} = 2 \angle 0^\circ \text{ V}$$

Solve for  $V_2$  by solving the node equation at node  $V_2$ :

$$\begin{aligned} \frac{V_1 - V_2}{-j} &= \frac{V_2}{1} + j \\ j(V_1 - 1) &= V_2(1 + j) \\ j &= V_2(1 + j) \\ V_2 &= \frac{j}{1 + j} \\ \mathbf{V}_2 &= \frac{\sqrt{2}}{2} \mathbf{e}^{j\frac{\pi}{4}} \text{ V} = \frac{\sqrt{2}}{2} \angle \frac{\pi}{4} \text{ V} \end{aligned}$$

Solve for  $V_3$  by solving the node equation at node  $V_3$ :

$$\begin{aligned} \frac{V_1 - V_3}{2} + j &= \frac{V_3}{j2} \\ j(V_1 - V_3) - 2 &= V_3 \\ j2 - 2 &= V_3(1 + j) \\ V_3 &= \frac{j2 - 2}{1 + j} = \frac{j4}{2} = 2e^{j\frac{\pi}{2}} \\ \mathbf{V}_3 &= 2\mathbf{e}^{j\frac{\pi}{2}} \text{ V} = 2 \angle \frac{\pi}{2} \text{ V} \end{aligned}$$

2. In the circuit shown for Problem 1, determine the loop-current phasors  $I_1$ ,  $I_2$ , and  $I_3$  and express them in polar form.

**Solution:**

Node loop equations:

$$\begin{aligned} (1) \quad j + I_2 &= I_3 \\ (2) \quad 2 - (-j)(I_1 - I_2) - 1(I_1 - I_3) &= 0 \\ (3) \quad 2 - 2I_2 - j2I_3 &= 0 \end{aligned}$$

Add 2\*(1) to (3)

$$2 + j2 - I_3(2 + j2) = 0$$

$$\mathbf{I}_3 = 1 \text{ A} = 1 \angle 0^\circ \text{ A}$$

Plug  $I_3$  into (1)

$$I_2 = 1 - j$$

$$\mathbf{I}_2 = \sqrt{2} \mathbf{e}^{-j\frac{\pi}{4}} \text{ A} = \sqrt{2} \angle \frac{-\pi}{4} \text{ A}$$

Plug  $I_2$  and  $I_3$  into (2)


$$2 + j(I_1 - 1 + j) - (I_1 - 1) = 0$$

$$2j + 1 = I_1(1 + j)$$


$$I_1 = \frac{2j + 1}{1 + j} = \frac{j + 3}{2}$$

$$\mathbf{I}_1 = \frac{\sqrt{10}}{2} \mathbf{e}^{j \tan^{-1}(1/3)} \text{ A} = \frac{\sqrt{10}}{2} \angle \tan^{-1}(1/3) \text{ A}$$

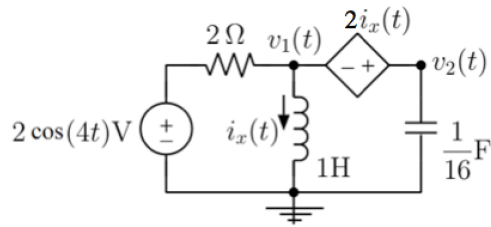3. Use the phasor method to determine  $v_1(t)$  in the following circuit:



**Solution:** In Phasor form:

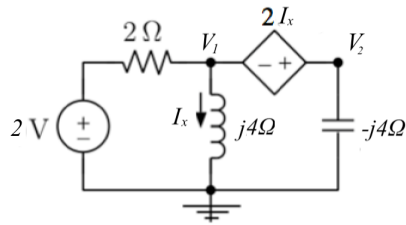

Equations:

$$(1) \frac{2 - V_1}{2} = \frac{V_1}{j4} + \frac{V_2}{-j4}$$

$$(2) V_1 + 2I_x = V_2$$

$$(3) I_x = \frac{V_1}{j4}$$

Plug (2) into (1):

$$\frac{2 - V_1}{2} = \frac{V_1}{j4} + \frac{V_1 + 2I_x}{-j4}$$

$$j2(2 - V_1) = V_1 - V_1 - 2I_x$$

Plug in value of  $I_x$  from (3)


$$j4 - j2V_1 = -2\frac{V_1}{j4}$$

$$-16 + 8V_1 = -2V_1$$

$$\frac{8}{5} = V_1$$

$$\mathbf{v}_1(\mathbf{t}) = \frac{8}{5} \cos(4\mathbf{t}) \text{ V}$$

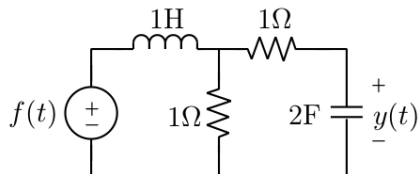4. In the following circuit, the input is  $f(t) = 4 - \cos(2t)$ . Determine the steady-state output  $y(t)$  of the circuit.




**Solution:** The input has two frequencies,  $\omega = 0$  rad/s and  $\omega = 2$  rad/s, so we have to use linearity to get

$$y(t) = y_0(t) + y_2(t)$$

For  $\omega = 0$  rad/s, in steady-state the inductor acts like a short and the capacitor as an open circuit, so that

$$y_0(t) = 4 \text{ V}$$

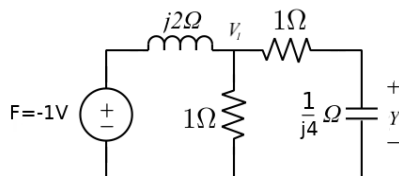For  $\omega = 2$  rad/s, the circuit in phasor form becomes



$$(1) Y = V_1 \frac{\frac{1}{j4}}{1 + \frac{1}{j4}} \text{ (Voltage Divider)}$$

$$(2) \frac{-1 - V_1}{j2} = \frac{V_1}{1} + \frac{V_1 - Y}{1}$$

Re-work (2):

$$\frac{-1 - V_1}{j2} = 2V_1 - Y$$

$$-1 - V_1 = j4V_1 - j2Y$$

$$j2Y - 1 = (j4 + 1)V_1$$

$$(1) \text{ can be re-written as: } Y(j4 + 1) = V_1$$

Plug in (1):

$$j2Y - 1 = (j4 + 1)(j4 + 1)Y$$

$$j2Y - 1 = (-15 + j8)Y$$


$$-1 = (-15 + j6)Y$$

$$Y = \frac{1}{15 - j6}$$

$$y_2(t) = 0.06 \cos(2t + 0.38) \text{ V}$$

$$\mathbf{y}(\mathbf{t}) = \mathbf{y}_0(\mathbf{t}) + \mathbf{y}_2(\mathbf{t}) = 4 + 0.06 \cos(2\mathbf{t} + 0.38) \text{ V}$$

5. Consider the network below:

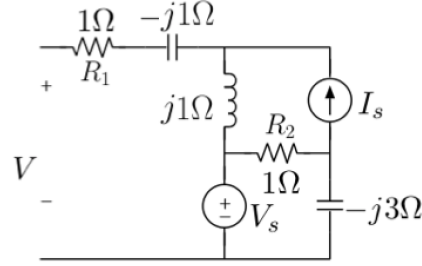

- (a) Determine the phasor  $V$  when  $I_s = 0$ .

**Solution:**  $\mathbf{V} = \mathbf{V}_s$  V

- (b) Determine the phasor  $V$  when  $V_s = 0$ .

**Solution:**  $\mathbf{V} = \mathbf{jI}_s$  V

- (c) Determine  $V$  when  $V_s = 4V$  and  $I_s = 2A$ , and calculate the average power absorbed in the resistors.

**Solution:**  $\mathbf{V} = \mathbf{4 - j2}$  V

$$V_{R1} = 0 \text{ V}$$

$$\mathbf{P}_{R1} = \mathbf{0} \text{ W}$$

$$\frac{V_s - V_1}{1} = I_s + \frac{V_1}{-j3}$$

$$\frac{4 - V_1}{1} = 2 + \frac{V_1}{-j3}$$

$$V_1 = \frac{6}{3 + j}$$

$$V_{R2} = V_s - V_1 = 4 - \frac{6}{3 + j} = \frac{6 + 4j}{3 + j}$$

$$P_{R2} = \frac{|V_{R2}|^2}{2R_2} = \frac{52}{10}$$

$$\mathbf{P}_{R2} = \frac{\mathbf{13}}{\mathbf{5}} = \mathbf{2.6} \text{ W}$$

- (d) What is the Thevenin equivalent and the available average power of the network when  $V_s = 4V$  and  $I_s = 2A$ ?

**Solution:**

$$\mathbf{V_T} = \mathbf{4 - j2} \text{ V}$$

$$\mathbf{Z_T} = \mathbf{1} \Omega$$

$$P_a = \frac{|V_T|^2}{8R_T} = \frac{20}{8}$$

$$\mathbf{P_a} = \mathbf{2.5} \text{ W}$$


6. Determine the impedance  $Z_L$  of a load that is matched to the following network at terminals a and b, and determine the net power absorbed by the matched load.

**Solution:**

$$V_1 = 2(2 + j3) = 4 + j6 \text{ V}$$

$$V_T = V_1 + j = 4 + j7 \text{ V}$$

$$Z_T = 4 + j3 \Omega$$

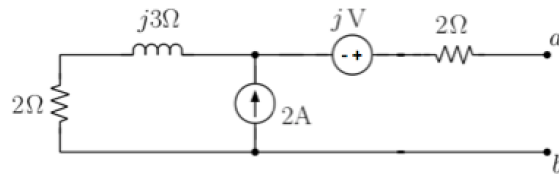


$$\mathbf{Z_L} = \mathbf{Z_T^*} = 4 - j3 \, \Omega$$

$$P_a = \frac{|V_T|^2}{8R_T} = \frac{65}{32}$$

$$\mathbf{P_a} = \mathbf{2.03 \, W}$$

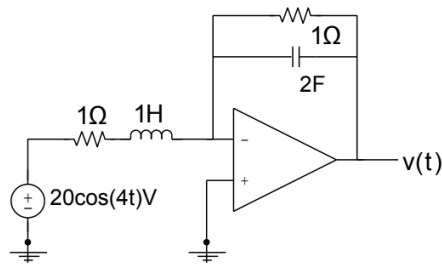7. Use the phasor method to determine the steady-state voltage  $v(t)$  in the following op-amp circuit. Please use ideal op-amp approximations.



**Solution:**

$$\frac{20}{1 + j4} = \frac{-V}{(1 + j8)^{-1}}$$

$$\frac{20}{1 + j4} = -V(1 + j8)$$

$$V = \frac{-20}{(1 + j4)(1 + j8)} = \frac{-20}{-31 - j12}$$

$$\mathbf{v(t) = 0.6\cos(4t + 0.37) \, V}$$