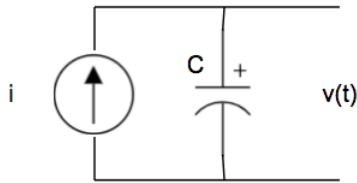


ECE210 / ECE211 - Homework 04
Solutions
Due date: Wednesday, Sep. 26, 2018

1. In the circuit shown below, let $C = 1\text{F}$ and $v(0^-) = 1\text{V}$. Determine $v(t)$ for $t > 0$ and sketch it.



Solution:

For capacitor C we have the following relation:

$$i(t) = C \times \frac{dV}{dt} \quad (1)$$


Given $C = 1\text{F}$ and initial condition $v(0^-) = 1\text{V}$,

$$\frac{dV}{dt} = \frac{1}{C} \times i(t) \quad (2)$$


$$\int_0^t \frac{dV}{d\tau} d\tau = \frac{1}{C} \int_0^t i(\tau) d\tau \quad (3)$$

$$\Rightarrow V(t) = 1 + \int_0^t i(\tau) d\tau \quad (4)$$

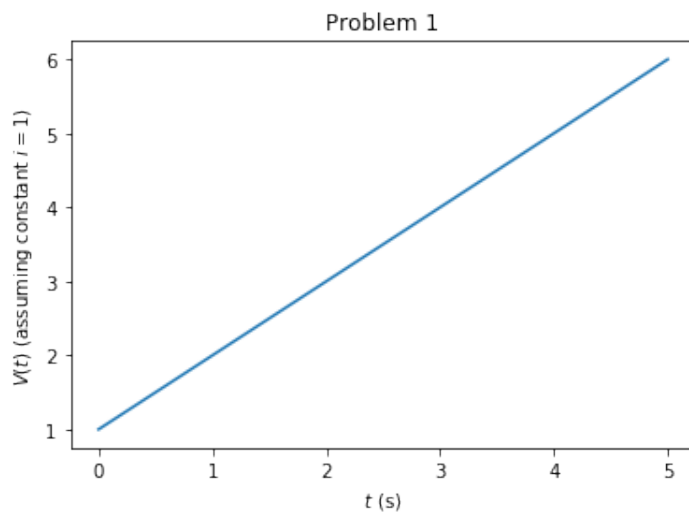For constant current i in this question, $V(t) = 1 + it$, and the plot is shown below.



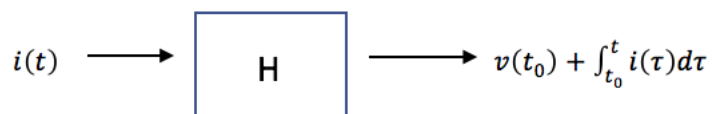2. Suppose we have the system below. Show that this system is zero-state linear.



Solution: For zero-state, $v(t_0) = 0$, so $v(t) = \int_{t_0}^t i(\tau) d\tau$.

$$i_1(t) \rightarrow v_1(t) = \int_{t_0}^t i_1(\tau) d\tau \quad (5)$$


$$i_2(t) \rightarrow v_2(t) = \int_{t_0}^t i_2(\tau) d\tau \quad (6)$$

$$i_3(t) = ai_1(t) + bi_2(t) \rightarrow v_3(t) = \int_{t_0}^t i_3(\tau) d\tau = \int_{t_0}^t [ai_1(\tau) + bi_2(\tau)] d\tau = a \int_{t_0}^t i_1(\tau) d\tau + b \int_{t_0}^t i_2(\tau) d\tau = av_1(t) + bv_2(t) \quad (7)$$

Therefore the system is zero-state linear.

3. The circuit shown below has been in DC steady state before the switch closes at $t = 0$ s.

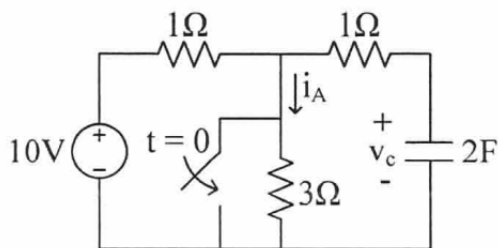- (a) Obtain $i_A(0^-)$, $i_A(0^+)$, $v_c(0^-)$ and $v_c(0^+)$.
- (b) Determine $i_A(t)$ for $t > 0$, and sketch it for $t > -1$.
- (c) Determine $v_c(t)$ for $t > 0$ and sketch it for $t > -1$.



Solution: (a)

$$i_A(0^-) = \frac{10 \text{ V}}{1\Omega + 3\Omega} = 2.5 \text{ A} \quad (8)$$

$$i_A(0^+) = \frac{10 \text{ V}}{1\Omega} + \frac{7.5 \text{ V}}{1\Omega} = 17.5 \text{ A} \quad (9)$$

$$v(0^-) = v(0^+) = 10 \text{ V} \cdot \frac{3\Omega}{1\Omega + 3\Omega} = 7.5 \text{ V} \quad (10)$$

(b) The general solution of $i_A(t)$ should take the following form

$$i_A(t) = A + Be^{-t/\tau} \quad (11)$$


where $\tau = R_{eq} \cdot C$ is the time constant of this RC circuit. First we find equivalent resistance $R_{eq} = 1\Omega$ by removing the voltage source, resulting $\tau = 2$.

Furthermore this general solution needs to satisfy the initial condition ($t = 0$) and the steady state condition ($t \rightarrow \infty$). plugging in those two numbers, we find

$$i_A(0^+) = A + B = 17.5 \quad (12)$$

$$i_A(\infty) = A = 10 \quad (13)$$
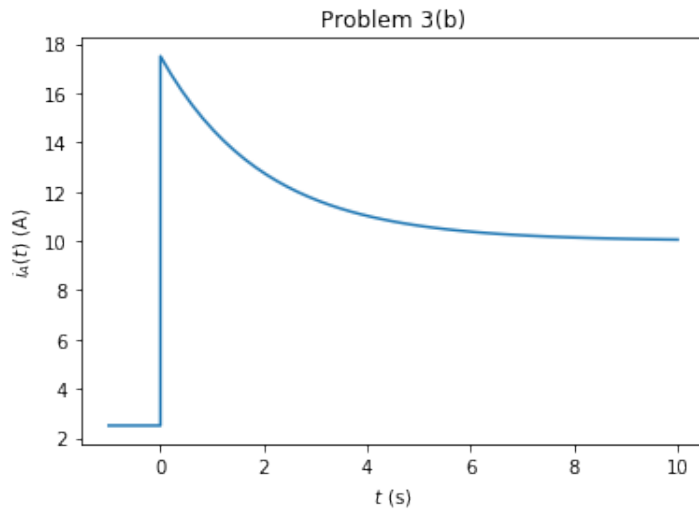
$$\implies i_A(t) = 10 + 7.5e^{-t/2} \quad (14)$$




(c) Similar to the procedures in (b), we first write down the general solution of $v(t)$ and solve for two unknowns:

$$v(t) = A + Be^{-t/2} \quad (15)$$

$$v(0^+) = A + B = 7.5 \quad (16)$$


$$v(\infty) = A = 0 \quad (17)$$
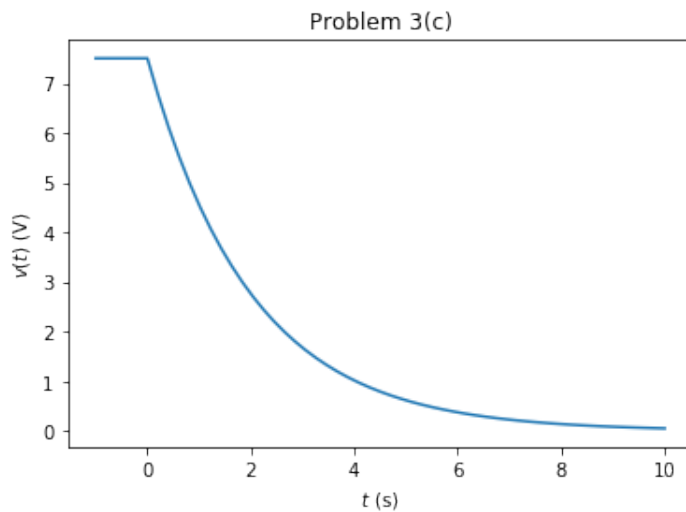
$$\Rightarrow v(t) = 7.5e^{-t/2} \quad (18)$$



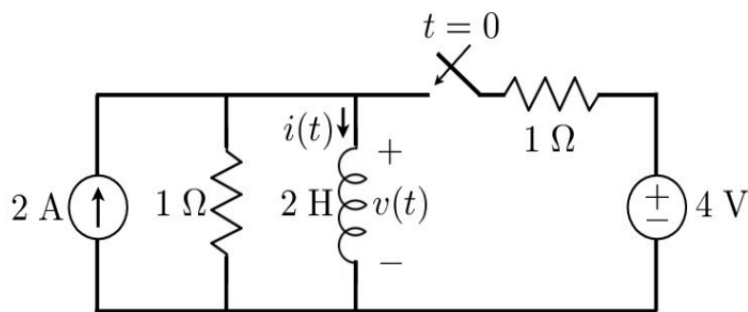4. The circuit shown below has been in DC steady state before the switch closes at $t = 0$.

- Obtain $i(0^-)$, $i(0^+)$, $v(0^-)$ and $v(0^+)$.
- Determine $i(t)$ for $t > 0$, and sketch it for $t > -1$.
- Determine $v(t)$ for $t > 0$ and sketch it for $t > -1$.



Solution: (a)

$$i_A(0^-) = i_A(0^+) = 2A \quad (19)$$

$$v(0^-) = 0V \quad (20)$$

$$v(0^+) = 2V \quad (21)$$


(b) The time constant for a RL circuit is $\tau = L/R_{eq} = 2H/\frac{1}{2}\Omega = 4s$, following the same procedures as in Problem 3, we find

$$i(t) = A + Be^{-t/4} \quad (22)$$

$$i(0^+) = A + B = 2 \quad (23)$$

$$i(\infty) = A = 2 + 4 = 6 \quad (24)$$
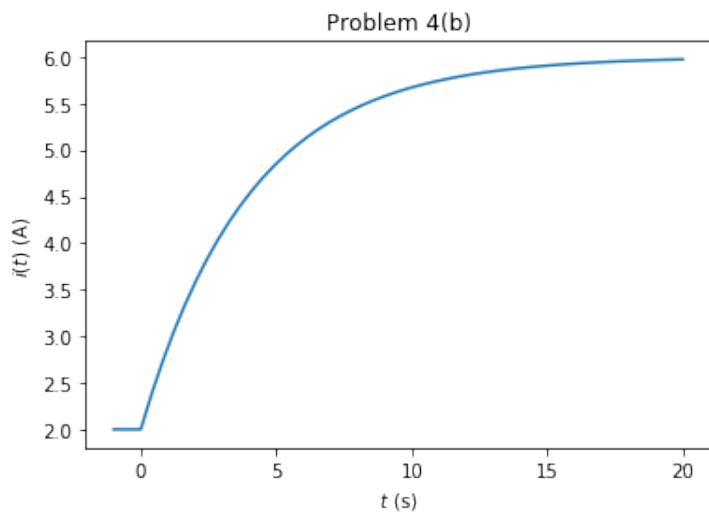
$$\Rightarrow i(t) = 6 - 4e^{-t/4} \quad (25)$$



(c) Similar to the procedures in (b), we first write down the general solution of $v(t)$ and solve for two unknowns:

$$v(t) = A + Be^{-t/4} \quad (26)$$

$$v(0^+) = A + B = 2 \quad (27)$$

$$v(\infty) = A = 0 \quad (28)$$

$$\Rightarrow v(t) = 2e^{-t/4} \quad (29)$$

