
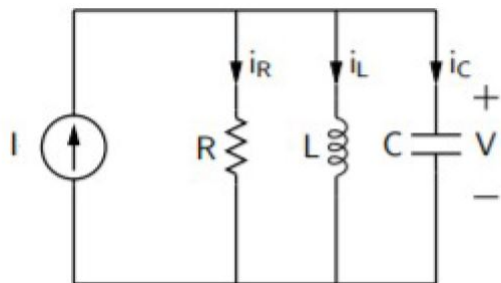


1. Consider the circuit drawn below:

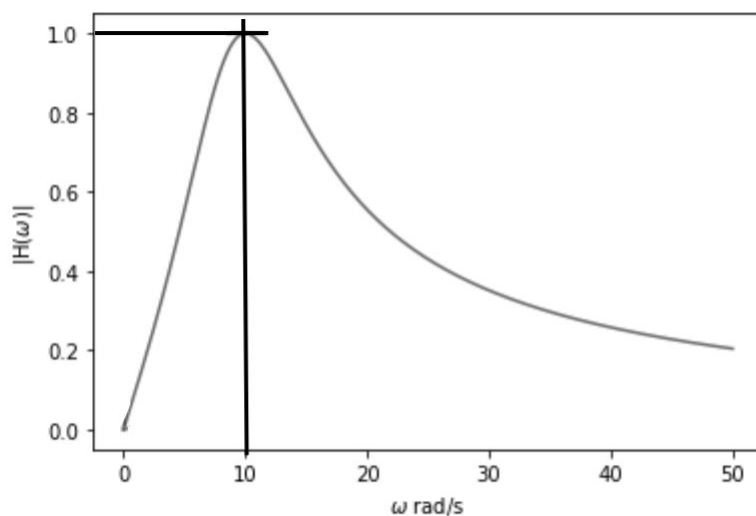


(a) $\omega = \frac{1}{\sqrt{LC}} = 10 \frac{rad}{s}$

(b) $H(\omega) = [\frac{1}{R} + \frac{1}{j\omega L} + j\omega C]^{-1}$




(c) See plots below:

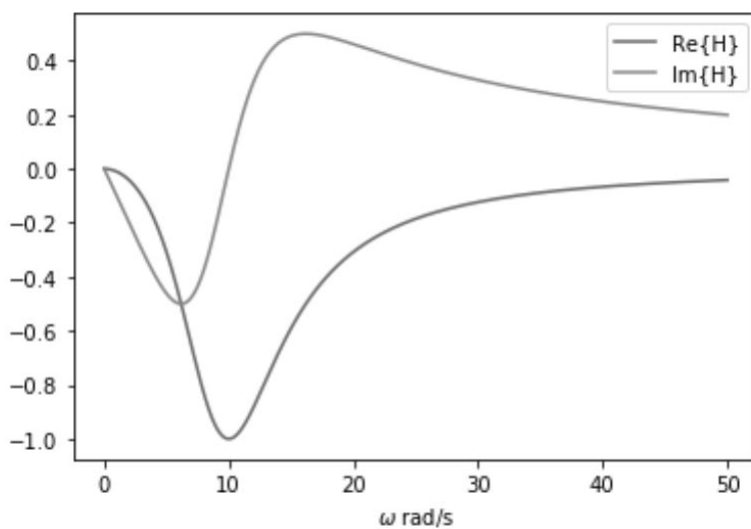


(d) The circuit acts as a band-pass filter because the signal with frequency away from 10rad/s will be attenuated (it has a gain close to 1 only for a small band of frequencies).

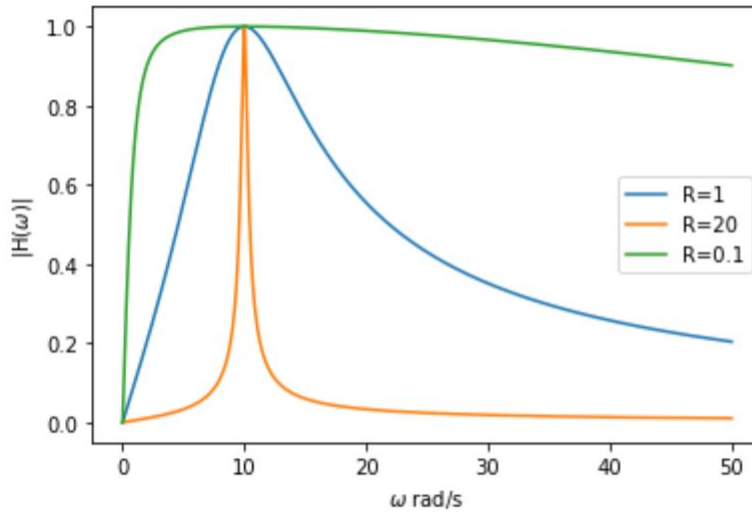(e) For both cases, we see that the resonant frequencies stay at 10rad/sec:



(f) From the plot above, we see that as the resistor value increase, the bandwidth decrease (narrower).

2. From the following circuit:

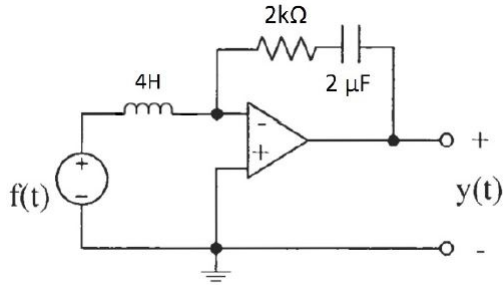

$$H(\omega) = \frac{Y}{F} = -\frac{2000 - \frac{5E5j}{\omega}}{4j\omega}$$


3. Given a linear system:

$$\frac{d^2 y}{dt^2} - 4 \frac{dy}{dt} + 4y(t) = \frac{df}{dt} + 2 \frac{d^2 f}{dt^2}$$

(a) $(j\omega)^2 - 4(j\omega)Y + 4Y = (j\omega)F + (j\omega)^2 2F$


$$H(\omega) = \frac{Y}{F} = \frac{j\omega - 2\omega^2}{-4j\omega - \omega^2 + 4}$$

(b) See plot below:

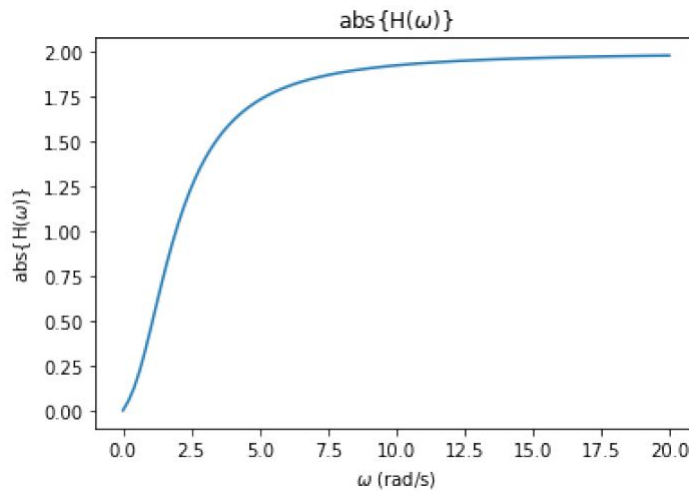

(c) High Pass Filter

(d) See plot below:

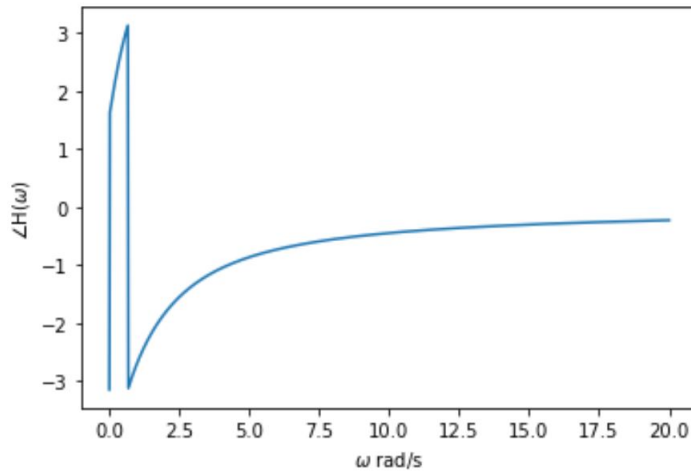


4. A linear system is given below:

$$\frac{d^2 y}{dt^2} - 6 \frac{dy}{dt} + 9y(t) = \frac{df}{dt}$$

(a) $(j\omega)^2 Y - 6(j\omega)Y + 9Y = (j\omega)F$


$$H(\omega) = \frac{Y}{F} = \frac{j\omega}{-6j\omega - \omega^2 + 9}$$

(b) See plot below:

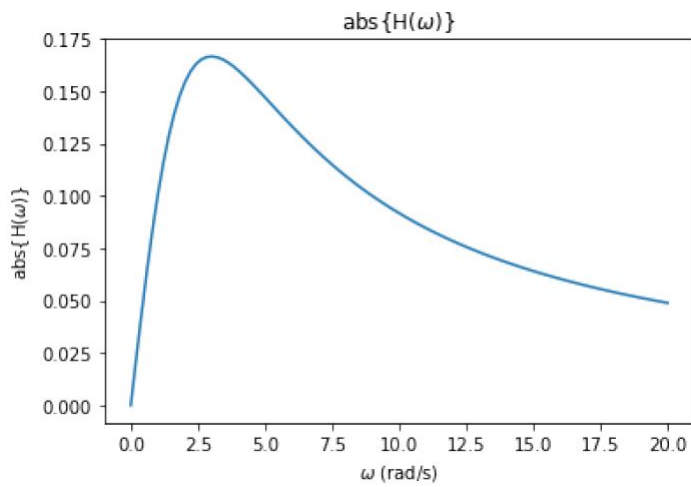


(c) Bandpass filter

(d) See plot below:

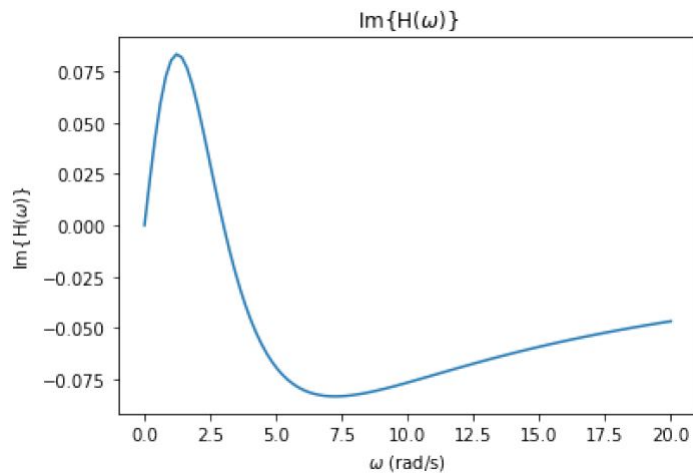


5. For circuit below:

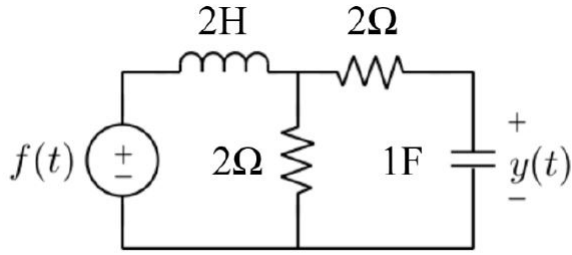

Given $f(t) = 4 - \cos(2t)$, we need to divide our analysis into DC and AC:

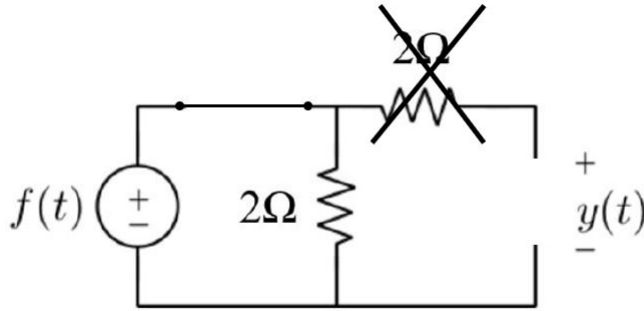(a) DC Analysis: $f(t)=4V$

At steady state: Inductor will act like a short whereas the capacitor will act like an open:



Therefore, $y(t) = 4$

(b) AC Analysis: $f(t)=-\cos(2t)$

Convert the whole circuit to a phasor and use KCL and VDR to find solution.

Using KCL:

$$\frac{-1-V_o}{j4} = \frac{V_o-Y}{2} + \frac{V_o}{2}$$

$$-1 = (1+j4)V_o - j2Y \quad (1)$$

Using VDR:

$$Y = V_o \left(\frac{\frac{1}{j2}}{2 + \frac{1}{j2}} \right) \quad (2)$$

Plugging (2) into (1) and we get:

$$-1 = (j8 - 15)Y - j2Y$$

$$Y = \frac{1}{15-j6} = 0.06 \angle 21.8^\circ$$

Combine DC and AC analysis and we get:

$$y(t) = 4 + 0.06 \cos(2t + 21.8^\circ)$$

6. We can express $f(t)$ as:

$$f(t) = 4\cos(2t) + 2\sin(t) + 2\cos(t) = 4\cos(2t) + 2\sqrt{2}\cos\left(t - \frac{\pi}{4}\right)$$

$$\text{With } H(\omega) = \frac{1-j\omega}{1+j\omega}$$

We get:

$$|H(1)| = 1 ; \angle H(1) = -1.57$$

$$|H(2)| = 1 ; \angle H(2) = -2.21$$

Therefore, we get:

$$y(t) = 2\sqrt{2}\cos\left(t - \frac{\pi}{4} - 1.57\right) + 4\cos(2t - 2.21)$$