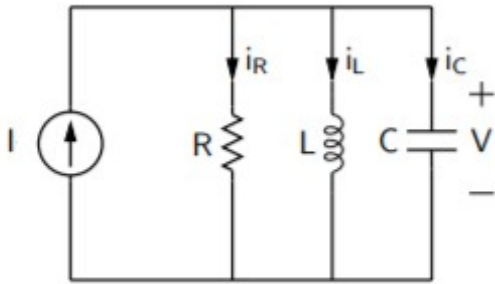


## ECE210/ ECE211

## Homework # 7


Due: Wednesday, October 17, by 6pm

1. Consider the circuit drawn below, where  $R = 1\Omega$ ;  $L = 0.1H$ ;  $C = 0.1 F$  and the frequency response of the circuit is:  $H(\omega) = V/I$ .



- (a) What is the resonant frequency of the circuit?
- (b) Plot  $|H(\omega)|$ , and label the resonant frequency on this plot. You may use Matlab, Mathematica, etc.
- (c) Plot  $\text{Re}\{H(\omega)\}$  and  $\text{Im}\{H(\omega)\}$ . You may use Matlab, Mathematica, etc.
- (d) Explain why this circuit might be called a “bandpass” filter.
- (e) Repeat (a) and (b) for resistor values of  $20\Omega$  and  $0.1\Omega$ .
- (f) Based on (d), how does the resistor value related the passband of the filter (e.g., does a large value for the resistor give a narrower or wide passband)?

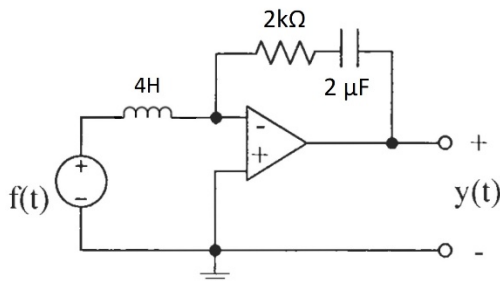2. Determine the frequency response of  $H(\omega)$  of the following circuit.



3. A linear system with input  $f(t)$  and output  $y(t)$  is described by the ODE

$$\frac{d^2 y}{dt^2} - 4 \frac{dy}{dt} + 4 y(t) = \frac{df}{dt} + 2 \frac{d^2 f}{dt^2}$$


- Determine the frequency response  $H(\omega)$  of the system.
- Determine and plot the magnitude response  $|H(\omega)|$  for  $0 < \omega < 20$  rad/s. You may use Matlab, Mathematica, etc.
- Determine if this filter is low pass, bandpass, highpass or none of these, and indicate why.
- Determine and plot the phase response  $\angle H(\omega)$  for  $0 < \omega < 20$  rad/s. You may use Matlab, Mathematica, etc.

4. A linear system with input  $f(t)$  and output  $y(t)$  is described by the ODE

$$\frac{d^2 y}{dt^2} - 6 \frac{dy}{dt} + 9 y(t) = \frac{df}{dt}$$

- Determine the frequency response  $H(\omega)$  of the system.
- Determine and plot the magnitude response  $|H(\omega)|$  for  $0 < \omega < 40$  rad/s. You may use Matlab, Mathematica, etc.
- Determine if this filter is low-pass, band-pass, highpass or none of these, and indicate why.
- Determine and plot the phase response  $\angle H(\omega)$  for  $0 < \omega < 40$  rad/s. You may use Matlab, Mathematica, etc.

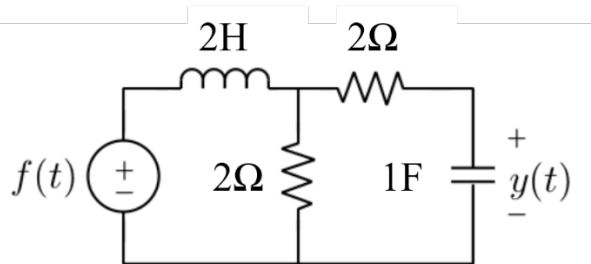5. In the following circuit, the input is  $f(t) = 4\cos(2t)$ . Determine the steady-state output  $y(t)$  of the circuit.



6. Given an input  $f(t) = 2e^{-j2t} + (1+j)e^{-jt} + (1-j)e^{jt} + 2e^{j2t}$  and  $H(\omega) = \frac{1-j\omega}{1+j\omega}$  determine the steady-state response  $y(t)$  of the system  $H(\omega)$  and express it as a real-valued signal.